

EXERCICES

UTILISATION DU PACKAGE `numeric_std`

- 1 Réaliser un additionneur 4 bits en instanciant l'additionneur 1 bit déjà présenté
- 2 Décrire un additionneur 4 bits en utilisant le package `numeric_std`
- 3 Décrire un soustracteur 4 bits en utilisant le package `numeric_std`
- 4 Décrire un comparateur 8 bits en utilisant le package `numeric_std`
- 5 Pour le comparateur 8 bits, est-il nécessaire de faire des conversions en `unsigned` ?

EXERCICE 1

SOLUTION

```
library ieee;
use ieee.std_logic_1164.all;
entity additionneur4bit is
port(
    a,b      : in  std_logic_vector(3 downto 0);
    cin      : in  std_logic;
    s        : out std_logic_vector(3 downto 0);
    cout     : out std_logic);
end;

architecture archConc of additionneur4bit is
component additionneur
port(
    a,b,cin  : in  std_logic;
    s,cout   : out std_logic);
end component;
signal c : std_logic_vector(2 downto 0);
begin
    add_1: additionneur port map (a(0),b(0),cin,s(0),c(0));
```

EXERCICE 1

SOLUTION

```
add_2: additionneur port map (a(1),b(1),c(0),s(1),c(1));  
add_3: additionneur port map (a(2),b(2),c(1),s(2),c(2));  
add_4: additionneur port map (a(3),b(3),c(2),s(3),cout);  
end archConc;
```

EXERCICE 2

SOLUTION

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity additionneur4bit_1 is
port(
    a,b      : in  std_logic_vector(3 downto 0);
    cin      : in  std_logic;
    s        : out std_logic_vector(3 downto 0);
    cout     : out std_logic);
end;

architecture archConc of additionneur4bit_1 is
    signal s_int : unsigned (4 downto 0);
    signal cin_nat: natural range 0 to 1;
begin
    cin_nat <= 1 when cin='1' else 0;
    s_int <= unsigned('0' & a) + unsigned('0' & b) + cin_nat;
    s      <= std_logic_vector(s_int(3 downto 0));
    cout   <= s_int(4);
end;
```

EXERCICE 2

SOLUTION

```
end archConc;
```

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity additionneur4bit_2 is
port(
    a,b      : in  std_logic_vector(3 downto 0);
    cin      : in  std_logic;
    s        : out std_logic_vector(3 downto 0);
    cout     : out std_logic);
end;

architecture archConc of additionneur4bit_2 is
    signal s_int : unsigned (4 downto 0);
    signal cin_vector: std_logic_vector (0 downto 0);
begin
    cin_vector(0) <= cin;
```

EXERCICE 2

SOLUTION

```
s_int <= unsigned('0' & a) + unsigned('0' & b) + unsigned("0000" &
cin_vector);
--s_int <= resize(unsigned(a),5) + resize(unsigned(b),5) +
resize(unsigned(cin_vector),5);
s      <= std_logic_vector(s_int(3 downto 0));
cout  <= s_int(4);
end archConc;
```

EXERCICE 3

SOLUTION

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity soustracteur4bit is
port(
    a,b      : in  std_logic_vector(3 downto 0);
    cin      : in  std_logic;
    s        : out std_logic_vector(3 downto 0);
    cout     : out std_logic);
end;

architecture archConc of soustracteur4bit is
    signal s_int : unsigned (4 downto 0);
    signal cin_vector: std_logic_vector (0 downto 0);
begin
    cin_vector(0) <= cin;
    s_int <= unsigned('0' & a) + unsigned(not('0' & b)) +
        unsigned("0000" & cin_vector);
    --s_int <= resize(unsigned(a),5) + resize(unsigned(b),5) +
        resize(unsigned(cin_vector),5);
end;
```

EXERCICE 3

SOLUTION

```
s      <= std_logic_vector(s_int(3 downto 0));  
cout   <= s_int(4);  
end archConc;
```

EXERCICE 4

SOLUTION

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity compareur8bit_1 is
port(
    a,b      : in  std_logic_vector(7 downto 0);
    eq,gt,lt : out std_logic);
end;

architecture archConc of compareur8bit_1 is
    signal diff: unsigned (7 downto 0);
begin
    diff <= unsigned(a)-unsigned(b);
    eq <= '1' when diff = 0 else '0';
    gt <= '1' when diff > 0 else '0';
    lt <= '1' when diff < 0 else '0';
end archConc;
```

EXERCICE 4

SOLUTION

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity compareur8bit is
port(
    a,b      : in  std_logic_vector(7 downto 0);
    eq,gt,lt : out std_logic);
end;

architecture archConc of compareur8bit is
begin
    eq <= '1' when a = b else '0';
    gt <= '1' when a > b else '0';
    lt <= '1' when a < b else '0';
end archConc;
```

EXERCICES DE SYNTHÈSE

CODAGE D'UNE ALU SIMPLE

- 1 Donnez un code permettant de synthétiser une ALU opérant sur des données de 8 bits et possédant les 5 modes suivants : ADD; SUB; AND; OR; XOR
- 2 Modifiez le code pour que la taille des données soit générique
- 3 Observez le résultat de synthèse dans la vue RTL
- 4 Écrivez et simulez cette ALU avec un testbench permettant de vérifier les 5 modes sur 4 vecteurs d'entrée chacun